

DIGITAL SYSTEMS

PRAKTIKUM 5



By:

Muhammad Irfan


NIM: L200184165

INFORMATION TECHNOLOGY

FACULTY OF COMMUNICATION AND INFORMATICS

UNIVERSITY OF MUHAMMADIYAH SURAKARTA

Experiment 1

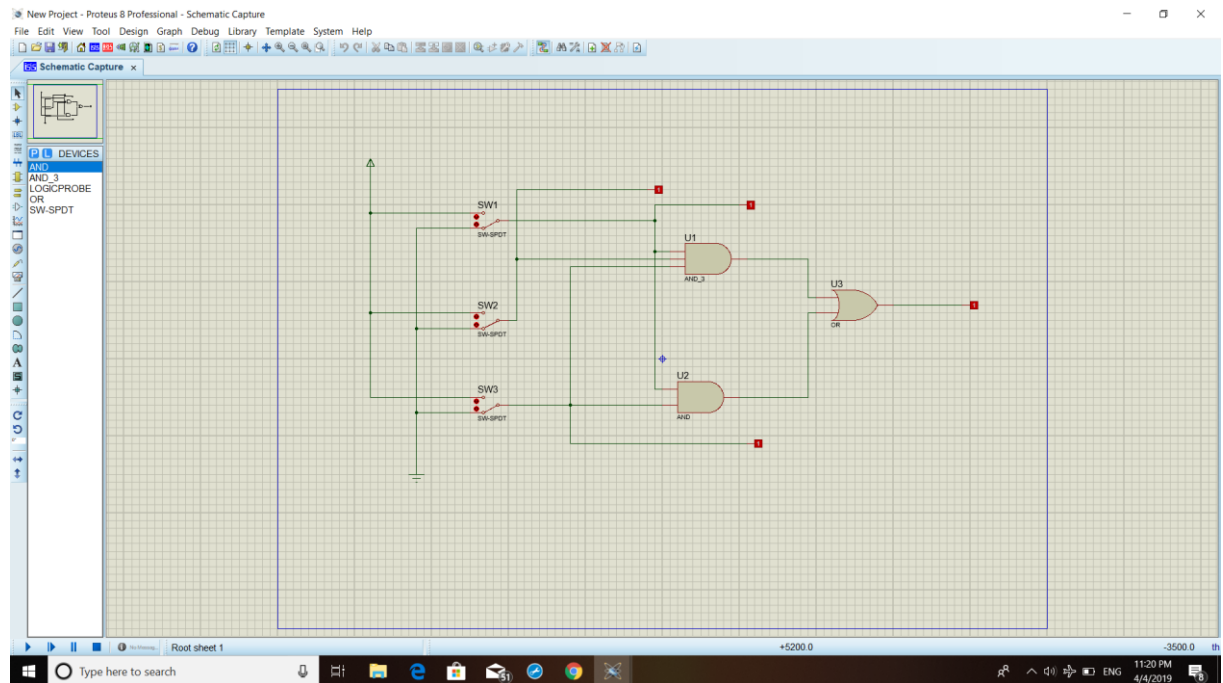

Picture 1.1. Logic gate combination

1. Boolean functions

$$F = ABC + AC$$

2. Truth table

A	B	C	F
0	0	0	0
1	0	0	0
0	1	0	0
1	1	0	0
0	0	1	0
1	0	1	1
0	1	1	0
1	1	1	1


3. Karnaugh map

		AB			
		00	01	11	10
C	0	0	0	0	0
	1	0	0	1	1

4. Boolean functions based on karnaugh map


$$F = AC$$

5. Logic gate combination based on new boolean functions

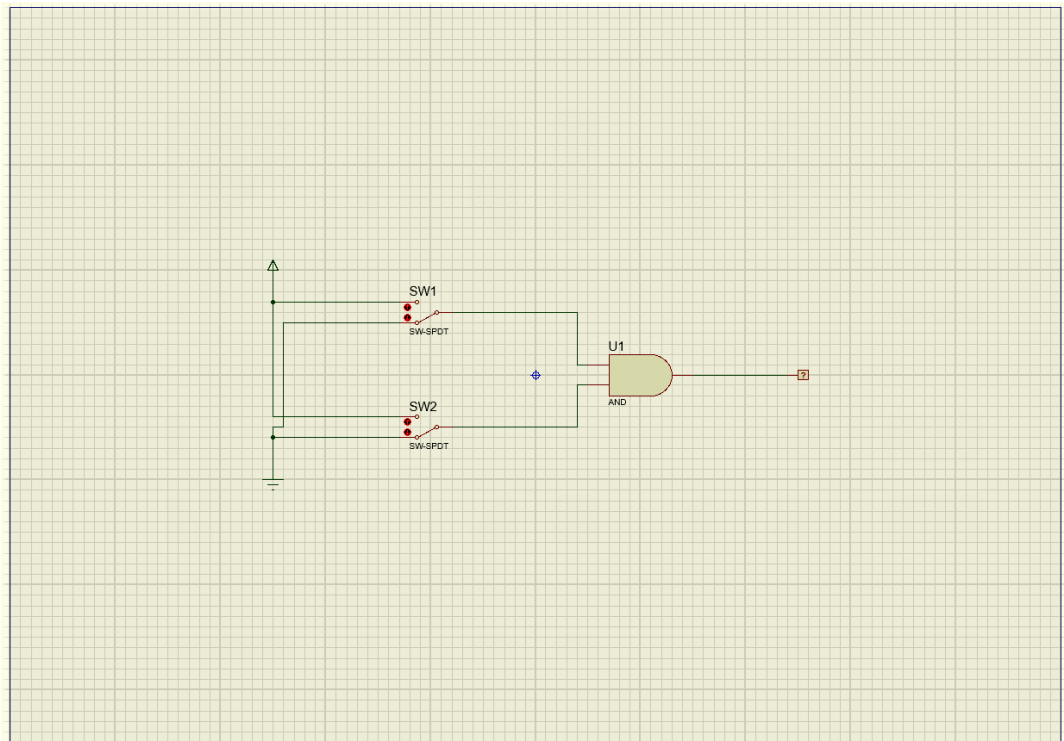

Picture 1.2. New logic gate combination

Experiment 2

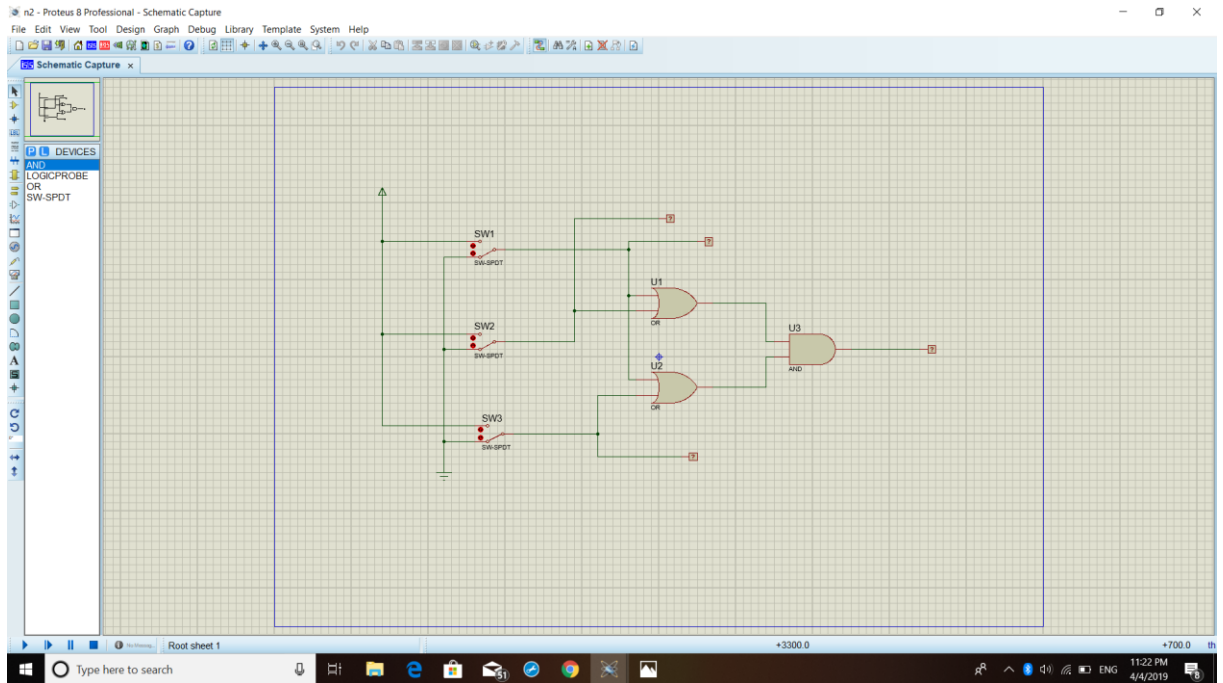

Picture 2.1. Logic gate combination

1. Boolean functions

$$F = ABC + AC$$

2. Truth table

A	B	C	F
0	0	0	0
1	0	0	1
0	1	0	0
1	1	0	1
0	0	1	0
1	0	1	1
0	1	1	1
1	1	1	1


3. Karnaugh map

		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	1

4. Boolean functions based on karnaugh map


$$A+BC$$

5. Logic gate combination based on new boolean functions

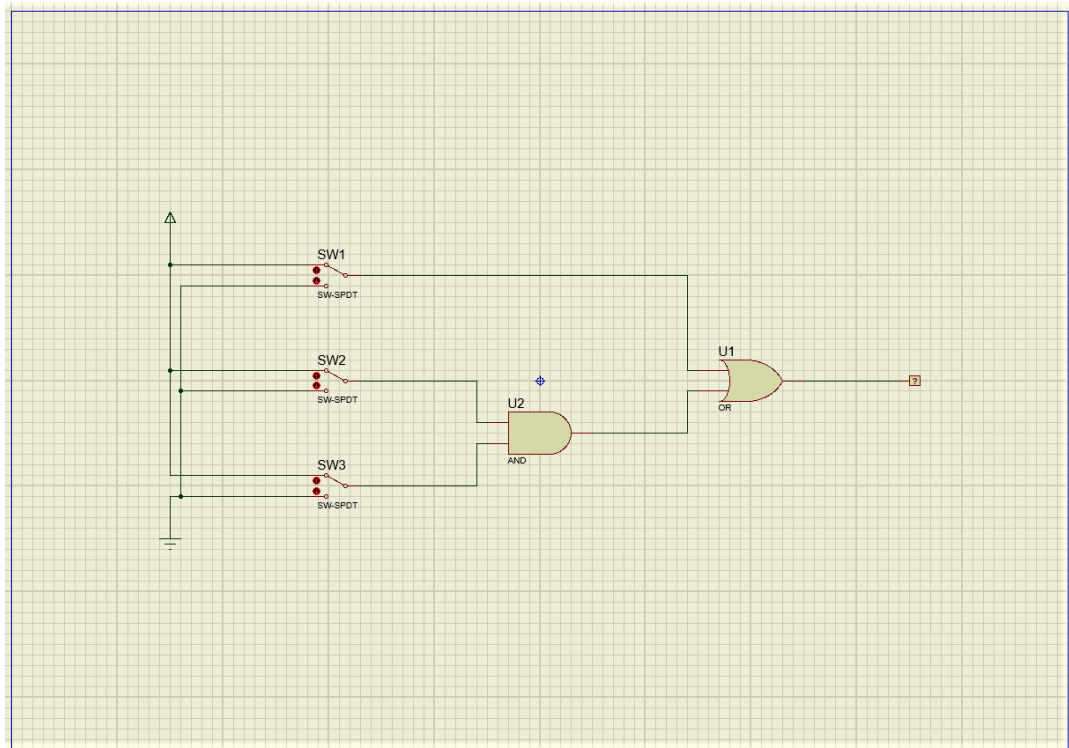

Picture 2.2. New logic gate combination

Experiment 3

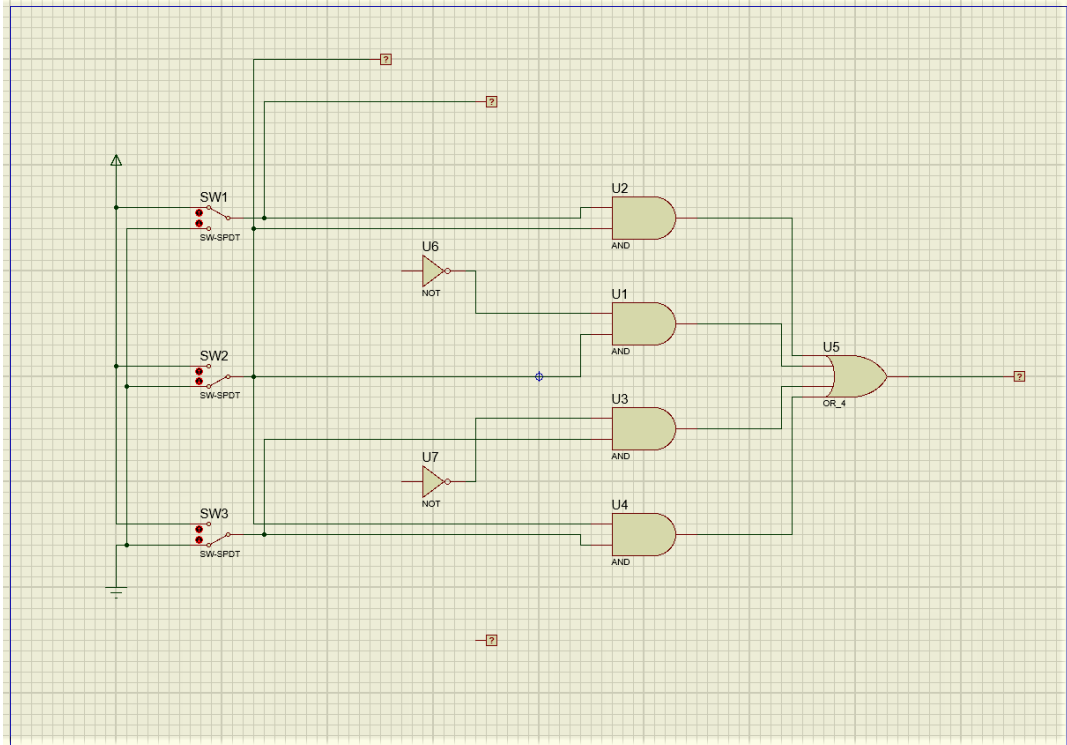

Picture 3.1. Logic gate combination

1. Boolean function

$$F = AB + A'B + B'C + BC$$

2. Truth table

A	B	C	F
0	0	0	0
1	0	0	0
0	1	0	1
1	1	0	1
0	0	1	1
1	0	1	1
0	1	1	1
1	1	1	1


3. Karnaugh map

		AB			
		00	01	11	10
C	0	0	1	1	0
	1	1	1	1	1

4. Boolean functions based on karnaugh map

$B+C$

5. Logic gate combination based on new boolean functions

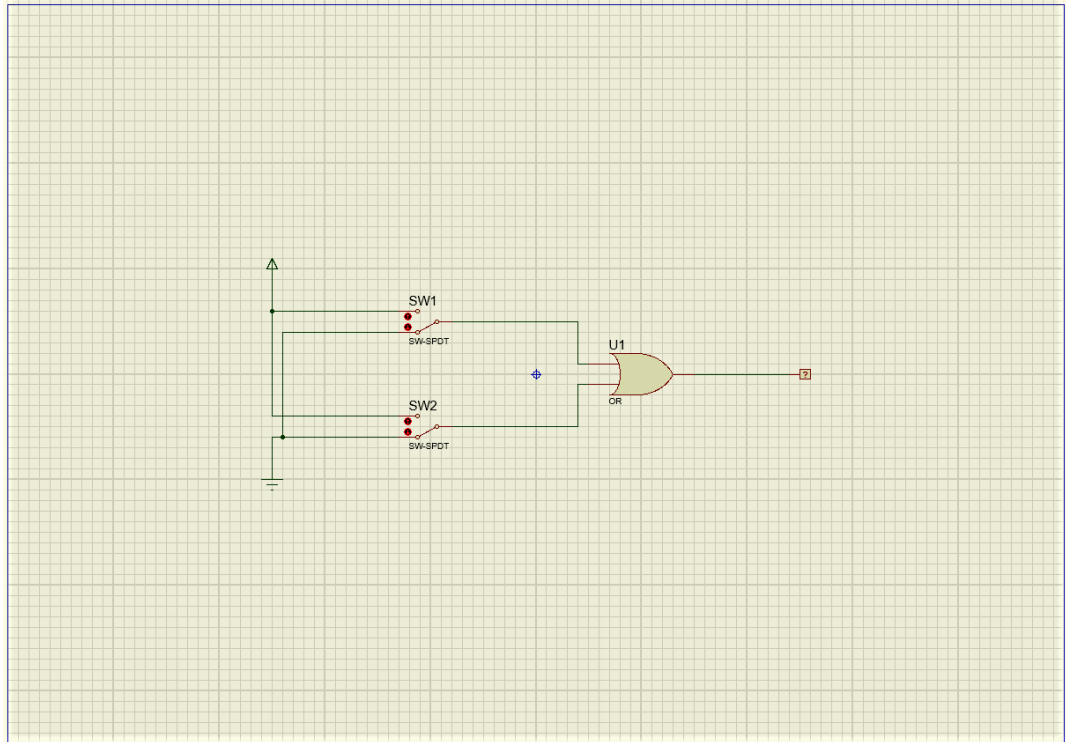

Picture 3.2. New logic gate combination