

**PRACTICUM SISDIG**

**MODUL 4**

**DIGITAL SYSTEM**



**By :**

**Muhammad Irfan**


**L200184165**

**INFORMATION TECHNOLOGY**

**FACULTY OF COMMUNICATION AND INFORMATICS**

**MUHAMMADIYAH UNIVERSITY OF SURAKARTA**

## Experiment 1

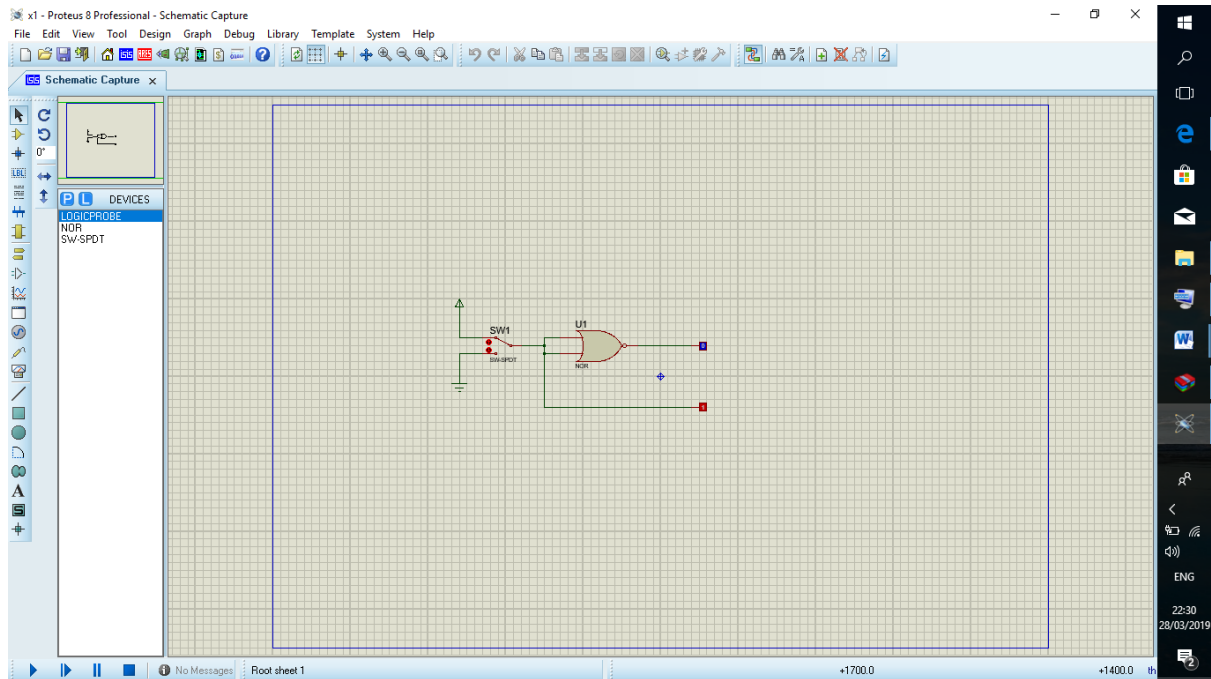

Picture 1.1 Gate 1 Variation

2. Boolean Function :  $L1 = \overline{L2} + L2 = \overline{L2}$

3. Truth Table :

SW1	SW2	L1
0	0	1
1	1	0


4. Time Diagram

L2	
L1	

5. Conclusion

NOR Gate in the picture above create a logic gate from NOT

## Experiment 2.

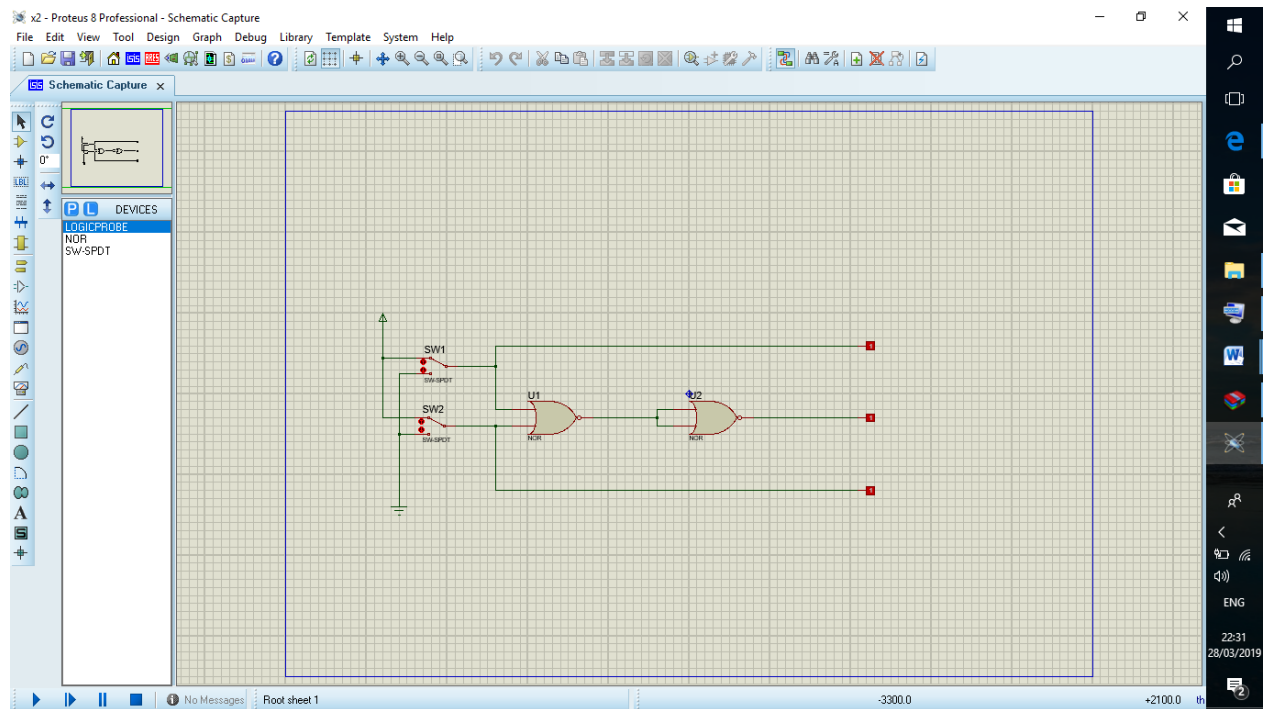


Picture 2.1 Gate 2 Variation

2. Boolean Function :  $L3 = \overline{L1 + L2} = L1 + L2$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	1


4. Time Diagram

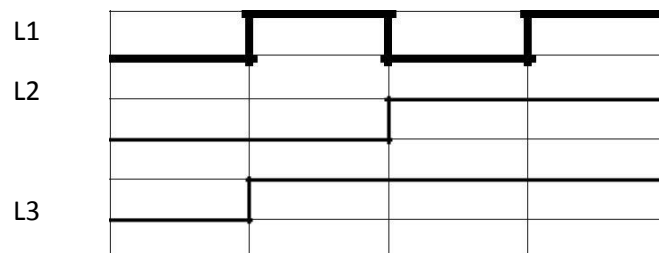

5. Conclusion

NOR Gate in the picture above create a logic from Gate Or

## Experiment 3

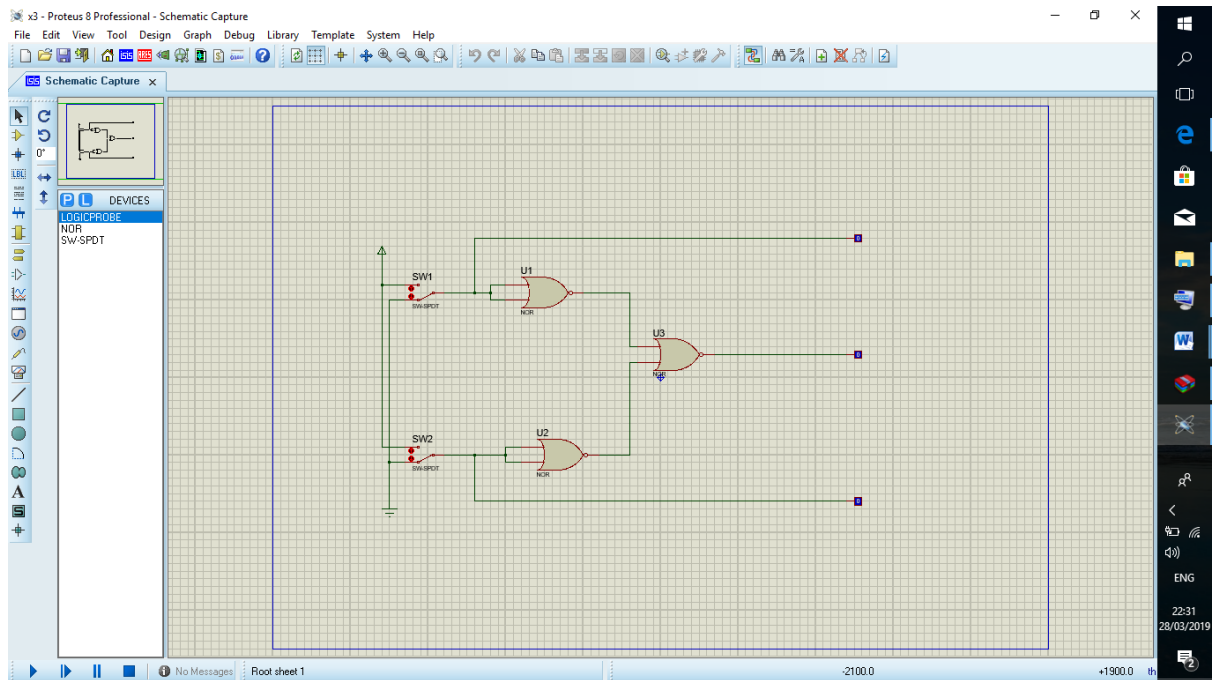


2. Boolean Function :  $L3 = L1 + L2 = L1 + L2$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
0	1	0	1	0
1	0	1	0	0
1	1	1	1	1


4. Time Diagram

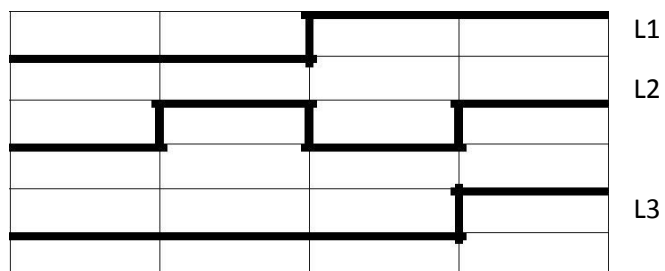

5. Conclusion

Gate NOR in the picture above create logic from Gate AND

## Experiment 4

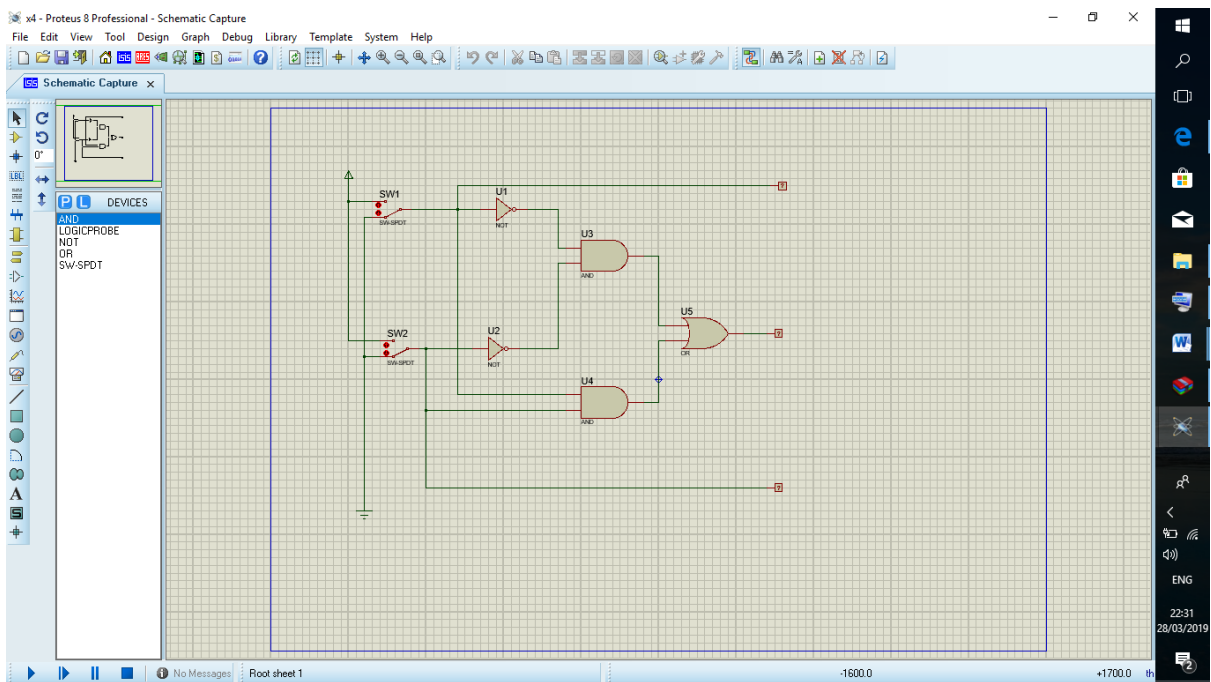

2. Boolean Function :  $L3 = L1 L2 + L1 L2 = L1 L2$

3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	1	1	1

4. Time Diagram


L1


L2

L3

5. Conclusion

Combination Gate in the picture above create logic from Gate XNORR

## Experiment 5

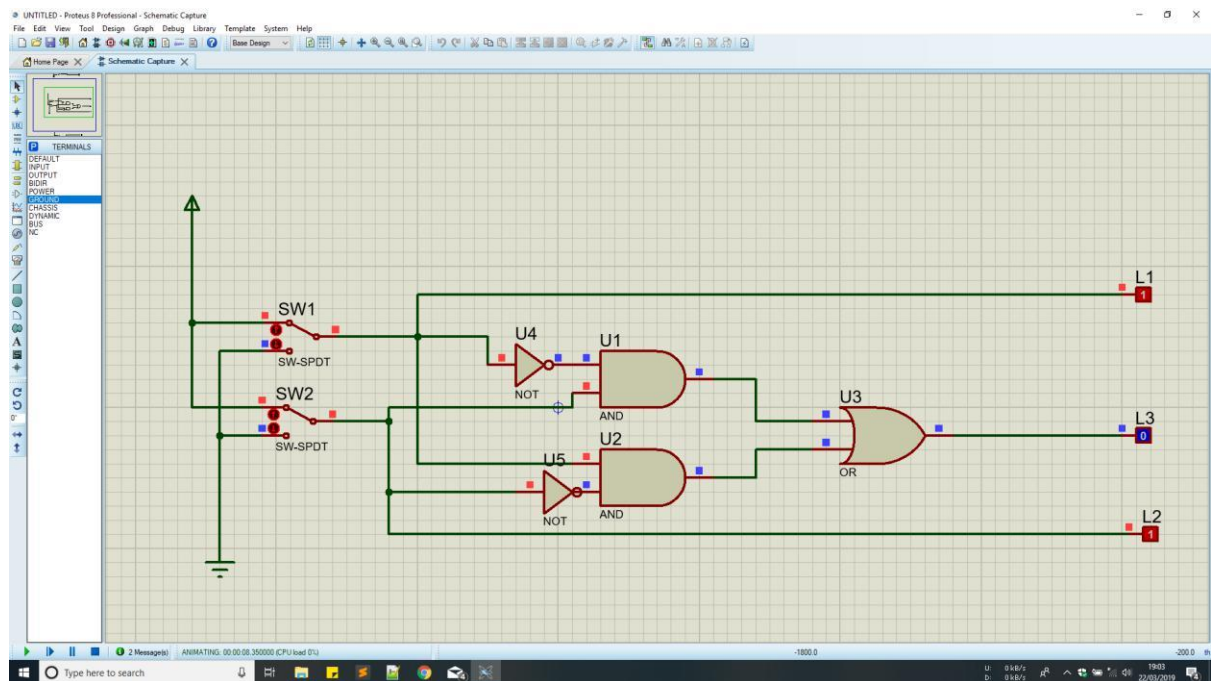

2. Boolean Function :  $L3 = \overline{L1}L2 + L1\overline{L2}$

### 3. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
0	1	0	1	1
1	0	1	0	1
1	1	1	1	0


#### 4. Time Diagram

				L1
				L2
				L3

## 5. Conclusion

Combinatio Gate in the picture above create logic from Gate XOR

## Additional Experiment 1.

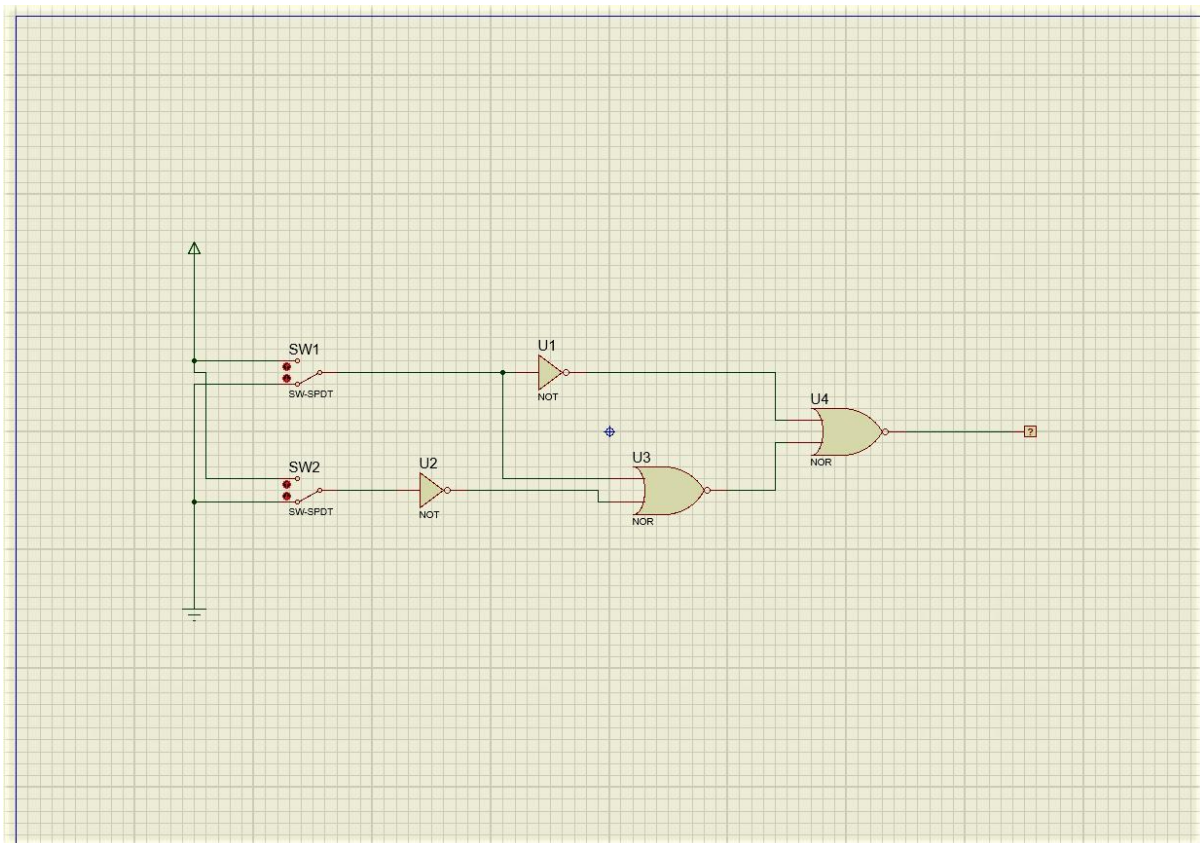

Picture 6.1. Set of gate

### 1. Truth Table

X	Y	F
0	0	0
0	1	0
1	0	1
1	1	1

### 2. Time Diagram


L1



### 3. Boolean Function

$$F = \neg(\neg X + \neg(X + \neg Y)) = X(X + \neg Y)$$

## Additional Experiment 2.

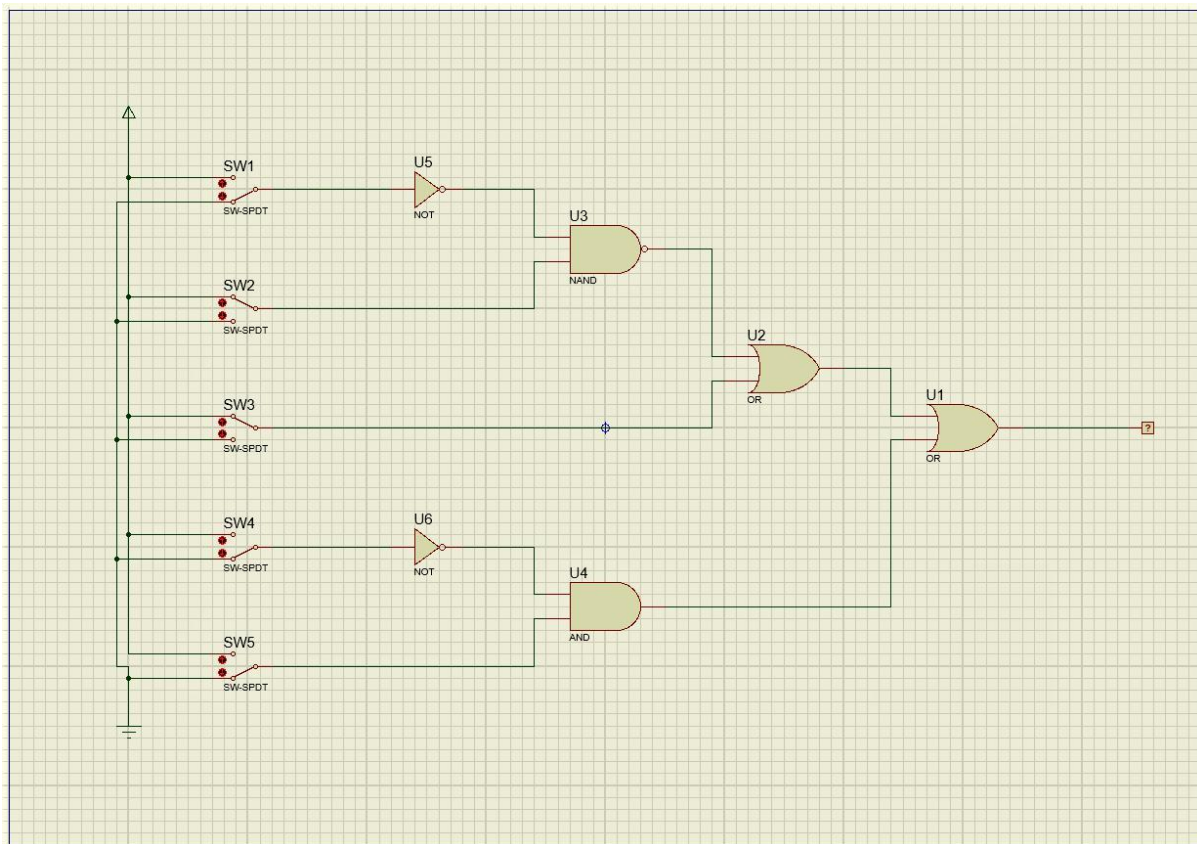

Picture 7.1. Set of gate for boolean function  $F = (\neg(\neg A.B) + C) + (\neg D.E)$